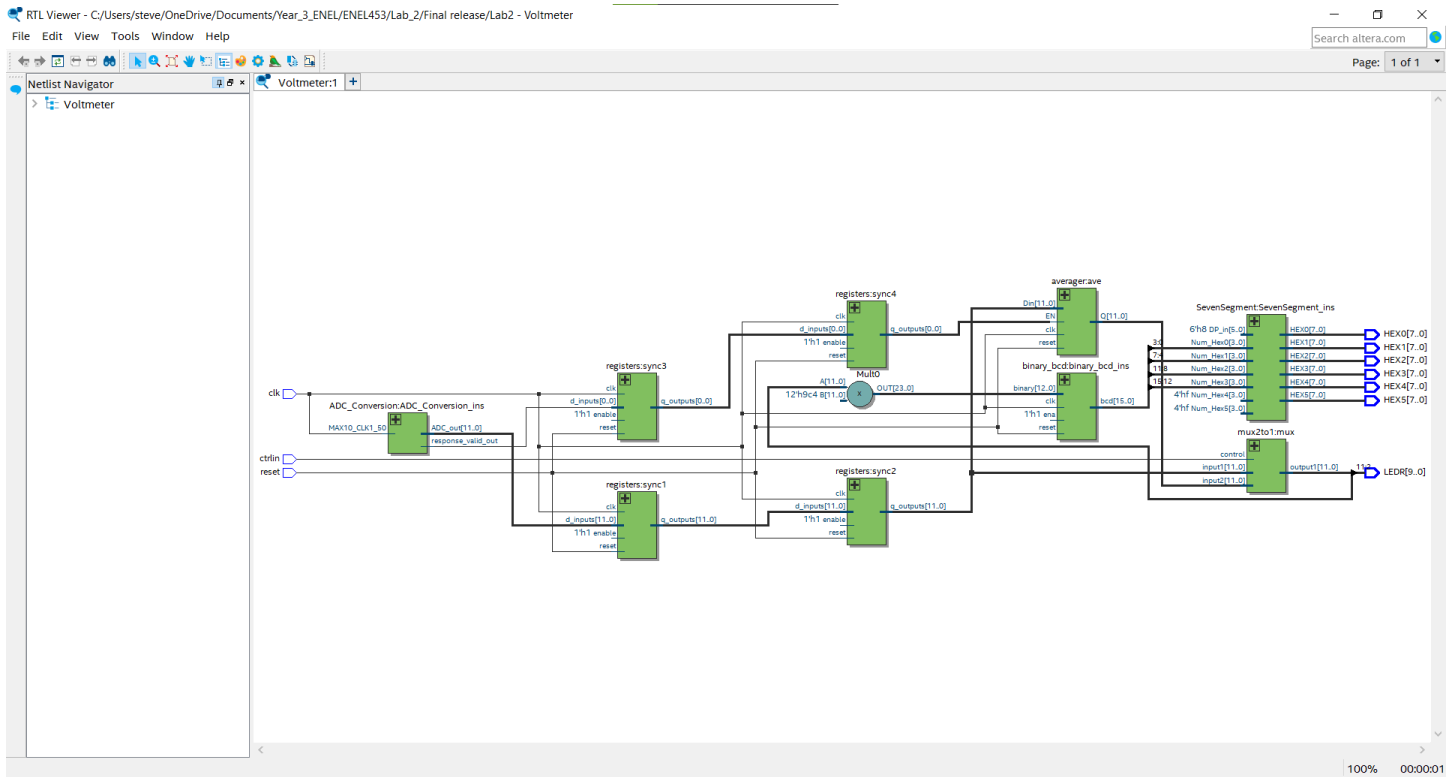


# ENEL 353 Lab 2


Group 13:

Frank Bustamante, Gustavo Da Costa-Gomez, Steven Poon and Patricia Sharleen

## Top level RTL Schematic



## Multiplexer Waveform:

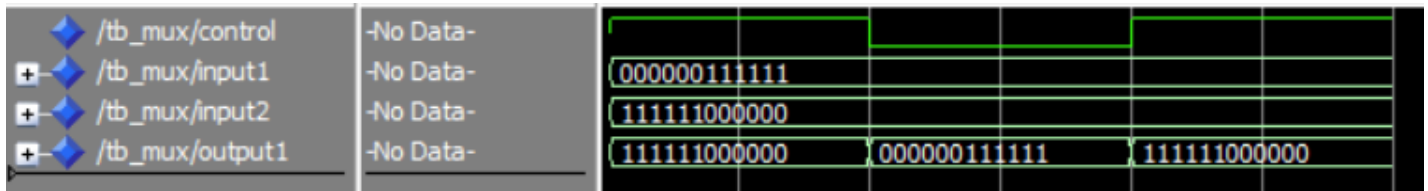

Continued next page

Voltmeter Waveform with Multiplexer:

